



CAMP SAVE-A-WATT™



CAMP CRAFT: Circuit Card

SUPPLIES NEEDED

- [Copper tape](#)
- [3V batteries](#)
- Push pin or safety pin
- [Light card template](#) printed on cardstock
- [LED lights](#)
- Scotch tape or folder labels
- Scissors

STEPS


1

Print the card template of your choice on cardstock and color.




2

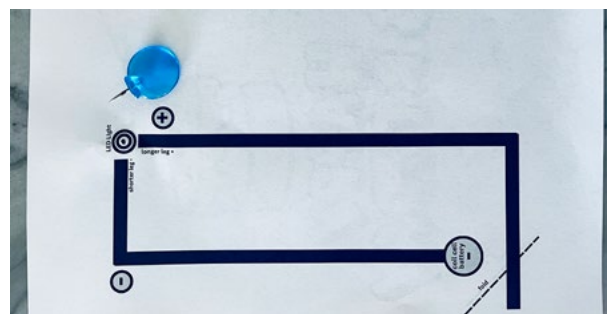Ask an adult to use a safety pin to poke a hole for the LED light.



3

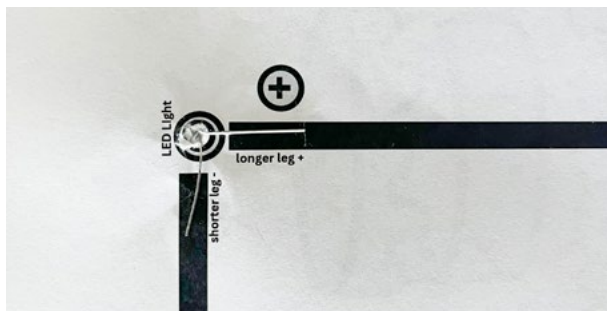Insert the LED and bend the LED legs flat on the back, following the diagram.




4

Add your copper tape covering the LED legs following the black pathway.



5

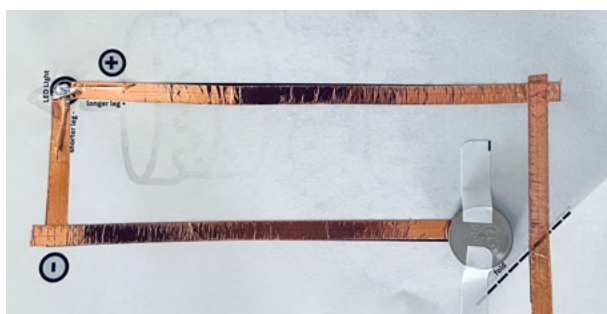Tape the battery (-) side down, leaving the top (+) side exposed for contact.



6

Fold on the dotted lines and press to turn on your card. Adjust the connection as needed.

